



INTERNATIONAL INSTITUTE OF
INFORMATION TECHNOLOGY

H Y D E R A B A D


VLSI PROJECT

Carry look ahead adder

Srujana Vanka
2020102005

 Question 1

To design a 4-bit carry look ahead (CLA) adder:



Proposed structure for the adder:

- To design a carry look ahead adder, I have used the static logic for all my blocks which have been implemented using basic gates.

The circuit can be divided mainly into 3 blocks:

1) Propagate and Generate block

Propagate and generate for the i th bit is given by:

$$\text{Propagate} = p_i = a_i \oplus b_i$$

$$\text{Generate} = g_i = a_i \cdot b_i$$

Propagate can be designed using 2 input XOR gates, whereas for Generate, we require 2 input AND gates.

2) Carry look ahead block (CLA)

Carry out (c_{i+1}) of the i th bit position can be written as (assuming $c_0 = 0$) follows:

$$\text{Carry} = c_{i+1} = (p_i \cdot c_i) + g_i, \text{ for } i = 1, 2, 3, 4$$

Carry out can be designed using 2,3,4 input AND and OR gates.


3) Sum block

Sum out (s_i) for the i th bit is given by:


Sum can be designed using 2 input XOR gates

$$\text{Sum} = s_i = p_i \oplus c_i$$

Circuit diagram for proposed structure:

 

Carry Look Ahead Adder

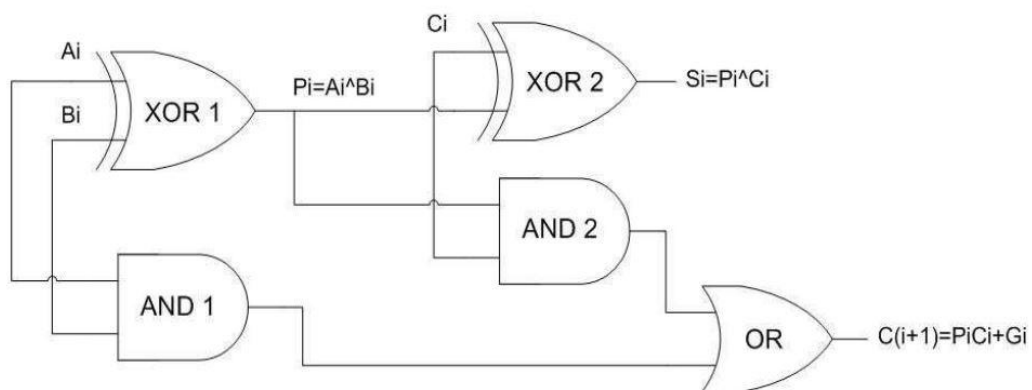

Question 2


Design details of each block

1) PROPAGATE AND GENERATE BLOCK

The propagate and generate for the i th bits is given by:

$$\text{Propagate} = p_i = a_i \oplus b_i$$
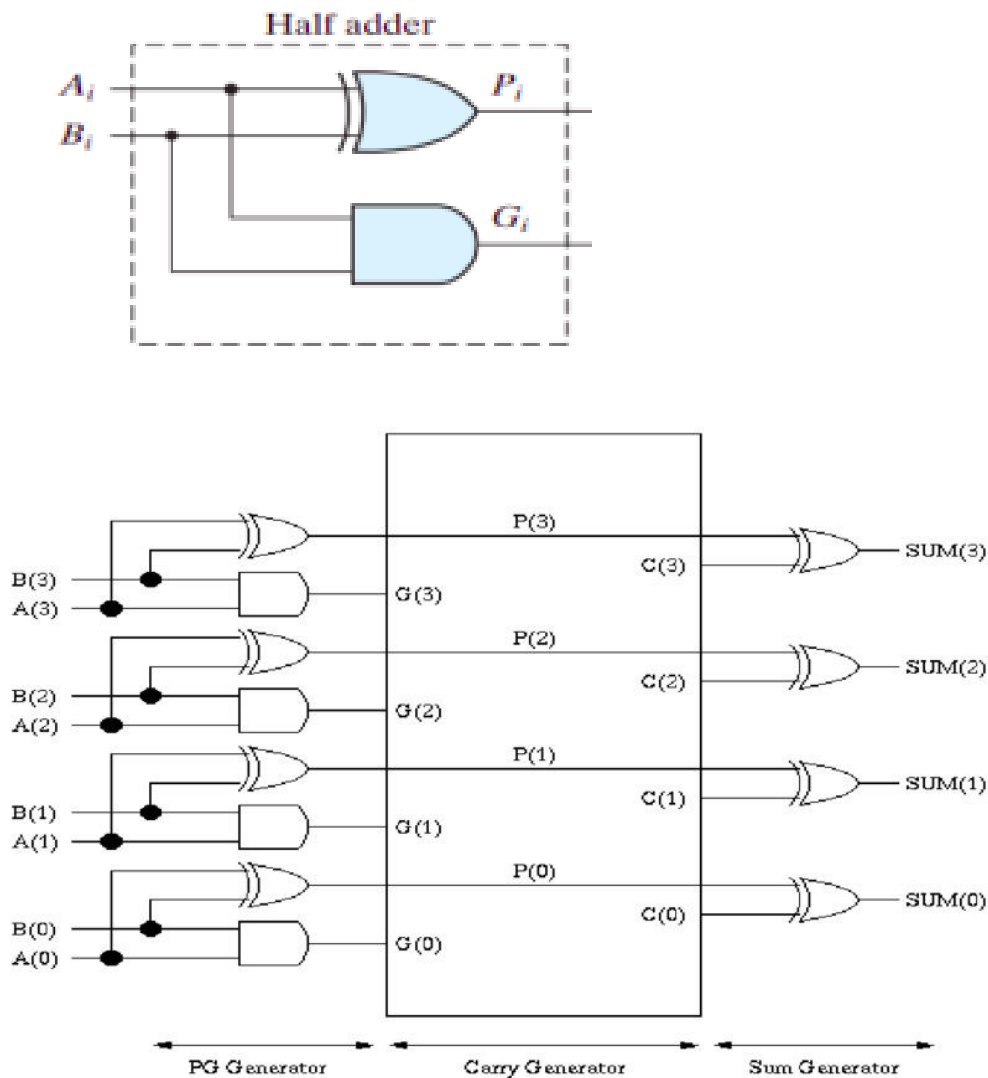
$$\text{Generate} = g_i = a_i \cdot b_i$$



2) CARRY LOOK AHEAD BLOCK

$$\text{Carry} = c_{i+1} = (p_i \cdot c_i) + g_i, \text{ for } i = 1, 2, 3, 4$$

Using the propagate and generate bits, we get the following:

For $c_{in} = 0$,


$$c_0 = 0 \text{ (given)}$$

$$c_1 = g_1$$

$$c_2 = p_2 g_1 + g_2$$

$$c_3 = p_3 p_2 g_1 + p_3 g_2 + g_3$$

 
$$c_{out} = p_4 p_3 p_2 g_1 + p_4 p_3 g_2 + p_4 g_3 + g_4$$




3) SUM BLOCK

The sum of the i th bit is given by:

$$s_i = p_i \oplus c_i$$

 


Carry Look Ahead Adder

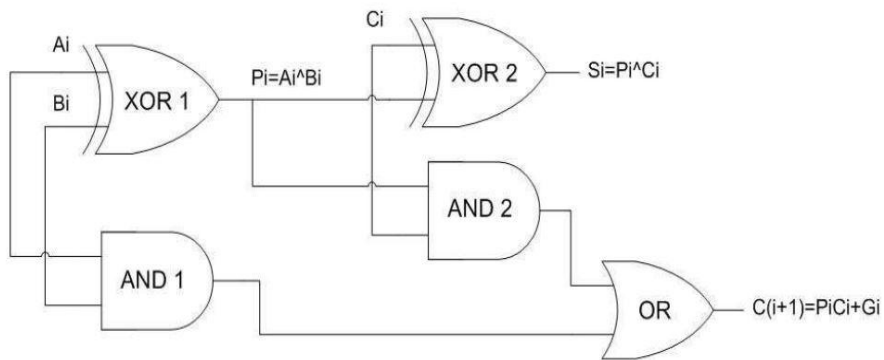


Adder modules


1) Propagate and generate block

 

2) Carry block

 

3) Sum block

 

- The lambda value is taken as $0.09u$ whereas $W = 10 * \lambda$

Question 3

NGSPICE simulations

- 2 input AND gate

```
*CMOS AND gate*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

* inputs
vin1 p gnd pulse (0 1.8 0 0.1n 0.1n 10n 20n)
vin2 q gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)

M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 r q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 r q s s CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M4 s p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M5 y r vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M6 y r gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
```



```

* delays
.tran 1n 120n

.measure tran trise
+ TRIG v(p) VAL = 0.9V RISE=1
+ TARG v(y) VAL = 0.9V RISE=1


.measure tran tfall
+ TRIG v(p) VAL = 0.9V FALL=1
+ TARG v(y) VAL = 0.9V FALL=1

.measure tran tpd param = '(trise + tfall)/2' goal=0

* outputs
.control
tran 1n 80n
run
plot v(y) v(p)+2 v(q)+4
.endc
.end

```

Output

 

- 3 input AND gate

```
*CMOS AND gate*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

* inputs
vin1 p 0 pulse (0 1.8 0 0.1n 0.1n 10n 20n)
vin2 q 0 pulse (0 1.8 0 0.1n 0.1n 20n 40n)
vin3 t 0 pulse (0 1.8 0 0.1n 0.1n 40n 80n)

M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 r q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 r t vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M4 r q s s CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M5 s t m m CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M6 m p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M7 y r vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}
```


```

M8 y r gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

* outputs
.control
tran 1n 100n
run
plot v(y) v(p)+2 v(q)+4 v(t)+6
.endc
.end

```

Output

 

- 4 input AND gate

```

*CMOS AND gate*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

* inputs

```

```

vin1 p 0 pulse (0 1.8 0 0.1n 0.1n 10n 20n)
vin2 q 0 pulse (0 1.8 0 0.1n 0.1n 20n 40n)
vin3 t 0 pulse (0 1.8 0 0.1n 0.1n 40n 80n)
vin4 x 0 pulse (0 1.8 0 0.1n 0.1n 80n 160n)

M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 r q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 r t vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M4 r x vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M5 r q s s CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M6 s t m m CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M7 m x n n CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M8 n p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M9 y r vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}


M10 y r gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

* outputs
.control
tran 1n 100n
run
plot v(y) v(p)+2 v(q)+4 v(t)+6 v(x)+8

```

```
.endc
.end
```

Output

 

- 2 input OR gate

```
*CMOS OR gate*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

* inputs
vin1 p gnd pulse (0 1.8 0 0.1n 0.1n 10n 20n)
vin2 q gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)

M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 s q r r CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
```

```

PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 s p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M4 s q gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}


M5 y s vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M6 y s gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

* outputs
.control
tran 1n 80n
run
plot v(y) v(p)+2 v(q)+4
.endc
.end

```

Output

 

- 3 input OR gate

```
*CMOS OR gate*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

* inputs
vin1 p gnd pulse (0 1.8 0 0.1n 0.1n 10n 20n)
vin2 q gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)
vin3 t 0 pulse (0 1.8 0 0.1n 0.1n 40n 80n)

M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 m q r r CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 s t m m CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M4 s p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M5 s q gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M5 s t gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M7 y s vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M8 y s gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
```


```

PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

* outputs
.control
tran 1n 80n
run
plot v(y) v(p)+2 v(q)+4 v(t)+6
.endc
.end

```

Output

 

- 4 input OR gate

```

*CMOS OR gate*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

* inputs

```



```

vin1 p gnd pulse (0 1.8 0 0.1n 0.1n 10n 20n)
vin2 q gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)
vin3 t 0 pulse (0 1.8 0 0.1n 0.1n 40n 80n)
vin4 x 0 pulse (0 1.8 0 0.1n 0.1n 80n 160n)

M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 m q r r CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 n t m m CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M4 s x n n CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M5 s p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M6 s q gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M7 s t gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M8 s x gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M9 y s vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}


M10 y s gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

* outputs
.control
tran 1n 80n
run
plot v(y) v(p)+2 v(q)+4 v(t)+6 v(x)+8

```

```
.endc
.end
```

Output

 

- XOR gate

```
*CMOS EXOR gate*

.include TSMC_180nm.txt
.include inverter.sub

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

* inputs
vin1 p gnd pulse (0 1.8 0 0.1n 0.1n 10n 20n)
vin2 q gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)

.subckt xor_subckt p q y vdd gnd

* inverter
```

```

M1 a p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 a p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M3 b q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M4 b q gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

* xor gate

M5 r b vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M6 y p r r CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M7 s q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M8 y a s s CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M9 m q y y CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M10 gnd p m m CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M11 n b y y CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M12 gnd a n n CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

.ends xor_subckt

xx1 p q y vdd gnd xor_subckt

```


```

* output
.control
tran 1n 80n
run
plot v(y) v(p)+2 v(q)+4

.endc
.end

```

Output

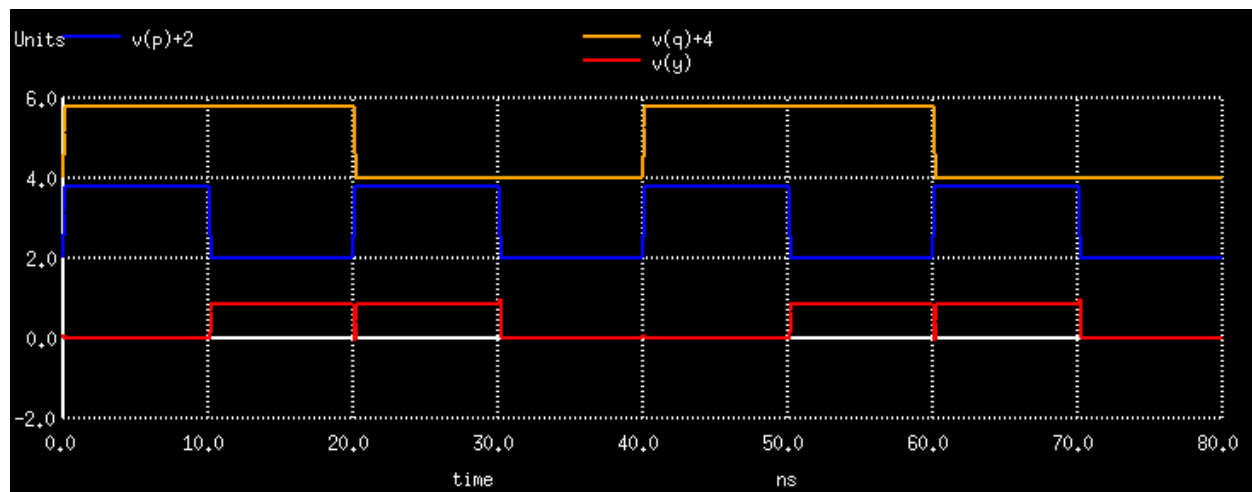

CLA BLOCK

- Propagate and generate block

```

*Propagate and generate block*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

```

```

vdd vdd gnd 'SUPPLY'

* Inputs
vin cin gnd pulse (0 1.8 0 0.1n 0.1n 160n 320n)

* Input A
vin_a1 a1 gnd pulse (0 1.8 0 0.1n 0.1n 10n 20n)
* vin_a2 a2 gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)
* vin_a3 a3 gnd pulse (0 1.8 0 0.1n 0.1n 40n 80n)
* vin_a4 a4 gnd pulse (0 1.8 0 0.1n 0.1n 80n 160n)

* Input B
vin_b1 b1 gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)
* vin_b2 b2 gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)
* vin_b3 b3 gnd pulse (0 1.8 0 0.1n 0.1n 40n 80n)
* vin_b4 b4 gnd pulse (0 1.8 0 0.1n 0.1n 80n 160n)

* XOR gate
.subckt xor_subckt p q y vdd gnd

* inverter
M1 a p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 a p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M3 b q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M4 b q gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

* xor gate
M5 r b vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M6 y p r r CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

```

```

M7 s q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M8 y a s s CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M9 m q y y CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M10 gnd p m m CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M11 n b y y CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M12 gnd a n n CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

.ends xor_subckt

* AND gate
.subckt and_subckt p q y vdd gnd

M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 r q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 r q s s CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M4 s p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M5 y r vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M6 y r gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

```

```

.ends

* Propagate and generate
xx1 a1 b1 p1 vdd gnd xor_subckt
xa1 a1 b1 g1 vdd gnd and_subckt

* xx2 a2 b2 p2 vdd gnd xor_subckt
* xa2 a2 b2 g2 vdd gnd and_subckt


* xx3 a3 b3 p3 vdd gnd xor_subckt
* xa3 a3 b3 g3 vdd gnd and_subckt

* xx4 a4 b4 p4 vdd gnd xor_subckt
* xa4 a4 b4 g4 vdd gnd and_subckt

* Output
.control
tran 1n 200n
run
plot v(p1) v(g1)+2 v(a1)+4 v(b1)+6
* plot v(p2) v(g2)
* plot v(p3) v(g3)
* plot v(p4) v(g4)
set curplottitle= "Srujana Vanka - 2020102005 - PGblock"
.endc
.end

```

Output

 

Delay:

Propagate $\approx 0.026\text{ns}$

Generate $\approx 0.041\text{ns}$

- Carry look ahead block

```
*Carry look ahead block*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param w = {10*LAMBDA}
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

* 2 input OR gate
.subckt or2_subckt p q y vdd gnd

M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 r q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 r q s s CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M4 s p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M5 y r vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M6 y r gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
```



```

.ends or2_subckt

* 3 input OR gate
.subckt or3_subckt p q t y vdd gnd
M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 m q r r CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 s t m m CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M4 s p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M5 s q gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M5 s t gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M7 y s vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M8 y s gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
.ends or3_subckt

* 4 input OR gate
.subckt or4_subckt p q t x y vdd gnd
M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 m q r r CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 n t m m CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

```

```

M4 s x n n CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M5 s p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M6 s q gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M7 s t gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M8 s x gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M9 y s vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M10 y s gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
.ends or4_subckt

* 2 input AND gate
.subckt and2_subckt p q y vdd gnd

M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 r q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M3 r q s s CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M4 s p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M5 y r vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

```

```
M6 y r gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}  
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}  
.ends and2_subckt
```

```
* 3 input AND gate
```

```
.subckt and3_subckt p q t y vdd gnd
```

```
M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}  
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}
```

```
M2 r q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}  
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}
```

```
M3 r t vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}  
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}
```

```
M4 r q s s CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}  
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
```

```
M5 s t m m CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}  
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
```

```
M6 m p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}  
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
```

```
M7 y r vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}  
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}
```

```
M8 y r gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}  
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}  
.ends and3_subckt
```

```
* 4 input AND gate
```

```
.subckt and4_subckt p q t x y vdd gnd
```

```
M1 r p vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}  
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}
```

```
M2 r q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}  
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}
```

```

M3 r t vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M4 r x vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M5 r q s s CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M6 s t m m CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M7 m x n n CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M8 n p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M9 y r vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M10 y r gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

.ends and4_subckt

```

```

*Carry look ahead block*

```

```

* C0 = 0

```

```

* c1 == g1

```

```

xxx p1 cin z__out vdd gnd and_subckt

```

```

xxx2 g1 z__out c1 vdd gnd or2_subckt

```

```

* C2 = p2g1 + g2

```

```

xa5 p2 g1 z2_out1 vdd gnd and_subckt

```

```

x01 g2 z2_out1 c2 vdd gnd or2_subckt

```

```

* C3 = p3p2g1 + p3g2 + g3

```

```

xa6 p3 p2 g1 z3_out2 vdd gnd and3_subckt

```

```

xa7 p3 p2 z2_out2 vdd gnd and_subckt

```

```

x02 g3 z3_out2 z2_out2 c3 vdd gnd or3_subckt

* c4 = p4p3p2g1 + p4p3g2 + p4g3 + g4
xa8 p4 p3 p2 g1 z4_out3 vdd gnd and4_subckt
xa9 p4 p3 g2 z3_out3 vdd gnd and3_subckt
xa10 p4 g3 z2_out3 vdd gnd and_subckt
x03 g4 z2_out3 z3_out3 z4_out3 c4 vdd gnd or4_subckt

* Output
.control
tran 1n 200n
run
set curplottitle= "Srujana Vanka - 2020102005 - carry"
.endc
.end

```

The delay of the carry look ahead block is around 0.24ns.

- Sum block

```

*Sum block*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param w = {10*LAMBDA}
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

* XOR gate
.subckt xor_subckt p q y vdd gnd

* inverter
M1 a p vdd vdd CMOSF W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

```

```

M2 a p gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M3 b q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M4 b q gnd gnd CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

* xor gate

M5 r b vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M6 y p r r CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M7 s q vdd vdd CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M8 y a s s CMOSP W={width_P} L={2*LAMBDA} AS={5*width_P*LAMBDA}
PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M9 m q y y CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M10 gnd p m m CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M11 n b y y CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M12 gnd a n n CMOSN W={width_N} L={2*LAMBDA} AS={5*width_N*LAMBDA}
PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

.ends xor_subckt

* Sum
* s1
xx5 p1 c1 s1 vdd gnd xor_subckt

```

```

* s2
xx6 p2 c2 s2 vdd gnd xor_subckt

* s3
xx7 p3 c3 s3 vdd gnd xor_subckt

* s4
xx8 p4 c4 s4 vdd gnd xor_subckt

* Output
.control
tran 1n 200n
run
plot v(s1) v(s2) v(s3) v(s4)
set curplottitle= "Srujana Vanka - 2020102005 - sum"
.endc
.end


```

The delay of the sum block is the same as the propagate (since both are XOR gates).



Question 4

Stick diagrams



- NOT gate

 


- NAND gate

  

- NOR gate

  


- XOR gate

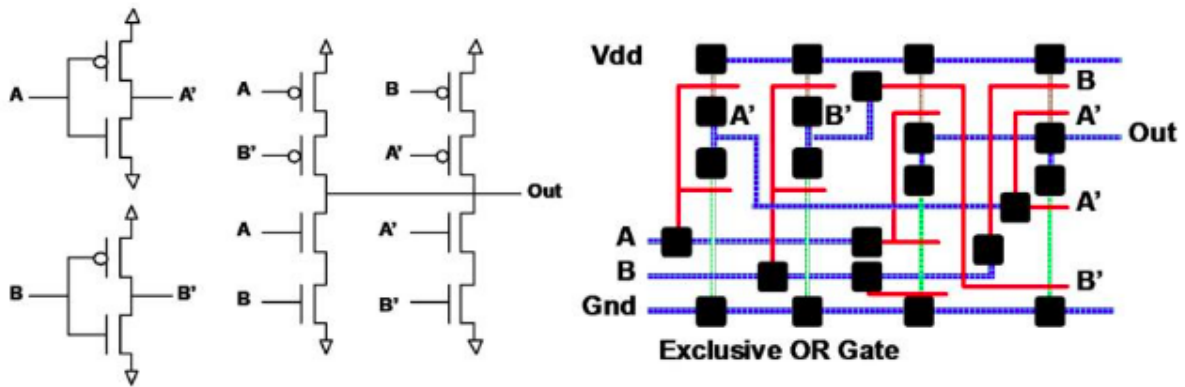


Question 5


NOT

 


2 INPUT AND

 


2 INPUT OR

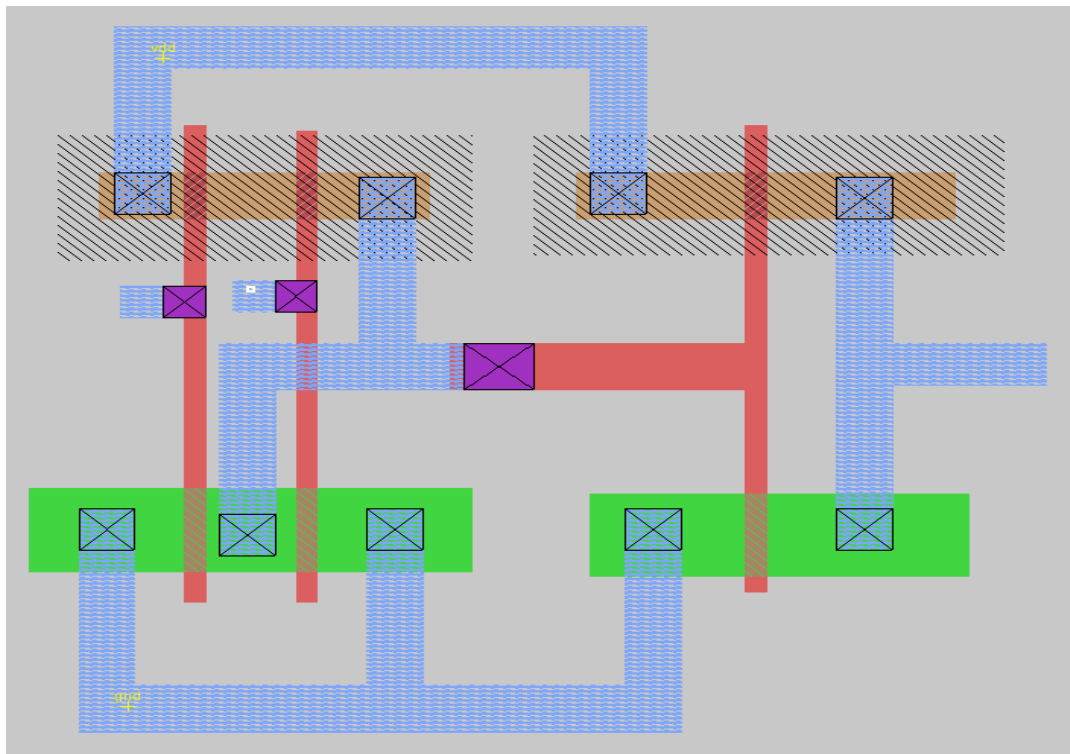


3 INPUT NAND

 


3 INPUT NOR

 


4 INPUT NAND

 

4 INPUT NOR

 

XOR

 

Propagate and generate block

```
* SPICE3 file created from pgblock.ext - technology: scmos
```

```
*Propagate and generate block*
```

```
.include TSMC_180nm.txt
```

```
.param SUPPLY=1.8
```

```
.param LAMBDA=0.09u
```

```
.param width_P={20*LAMBDA}
```

```
.param width_N={10*LAMBDA}
```

```
.global gnd vdd
```

```
vdd vdd gnd 'SUPPLY'
```

```
* Inputs
```

```
vin cin gnd pulse (0 1.8 0 0.1n 0.1n 160n 320n)
```

```
* Input A
```

```
vin_a1 a1 gnd pulse (0 1.8 0 0.1n 0.1n 10n 20n)
```

```
vin_a11 a11 gnd pulse (1.8 0 0 0.1n 0.1n 10n 20n)
```

```

vin_a2 a2 gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)
vin_a21 a21 gnd pulse (1.8 0 0 0.1n 0.1n 20n 40n)
vin_a3 a3 gnd pulse (0 1.8 0 0.1n 0.1n 40n 80n)
vin_a31 a31 gnd pulse (1.8 0 0 0.1n 0.1n 40n 80n)
vin_a4 a4 gnd pulse (0 1.8 0 0.1n 0.1n 80n 160n)
vin_a41 a41 gnd pulse (1.8 0 0 0.1n 0.1n 80n 160n)

* Input B
vin_b1 b1 gnd pulse (0 1.8 0 0.1n 0.1n 10n 20n)
vin_b11 b11 gnd pulse (1.8 0 0 0.1n 0.1n 10n 20n)
vin_b2 b2 gnd pulse (0 1.8 0 0.1n 0.1n 20n 40n)
vin_b21 b21 gnd pulse (1.8 0 0 0.1n 0.1n 20n 40n)
vin_b3 b3 gnd pulse (0 1.8 0 0.1n 0.1n 40n 80n)
vin_b31 b31 gnd pulse (1.8 0 0 0.1n 0.1n 40n 80n)
vin_b4 b4 gnd pulse (0 1.8 0 0.1n 0.1n 80n 160n)
vin_b41 b41 gnd pulse (1.8 0 0 0.1n 0.1n 80n 160n)
.option scale=0.09u

M1000 and_cla_0/vdd xor_cla_0/a_25_n47# xor_cla_0/a_6_19#
xor_cla_0/w_n72_13# pfet w=19 l=4
+ ad=4404 pd=1144 as=361 ps=76
M1001 xor_cla_0/a_n61_n43# xor_cla_0/a_25_n47# and_cla_0/gnd Gnd nfet w=12
l=4
+ ad=768 pd=200 as=3516 ps=1048
M1002 xor_cla_0/a_n40_n43# xor_cla_0/a_n22_n46# xor_cla_0/a_n40_19#
xor_cla_0/w_n72_13# pfet w=19 l=4
+ ad=380 pd=78 as=342 ps=74
M1003 xor_cla_0/a_n40_19# xor_cla_0/a_n49_n11# and_cla_0/vdd
xor_cla_0/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1004 xor_cla_0/a_6_19# xor_cla_0/a_2_n49# xor_cla_0/a_n40_n43#
xor_cla_0/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1005 xor_cla_0/a_n61_n43# xor_cla_0/a_n22_n46# xor_cla_0/a_n40_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=216 ps=60
M1006 and_cla_0/gnd xor_cla_0/a_2_n49# xor_cla_0/a_n61_n43# Gnd nfet w=12
l=4
+ ad=0 pd=0 as=0 ps=0
M1007 xor_cla_0/a_n40_n43# xor_cla_0/a_n49_n11# xor_cla_0/a_n61_n43# Gnd

```

```

nfet w=12 l=4
+ ad=0 pd=0 as=0 ps=0
M1008 and_cla_0/vdd xor_cla_1/a_25_n47# xor_cla_1/a_6_19#
xor_cla_1/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=361 ps=76
M1009 xor_cla_1/a_n61_n43# xor_cla_1/a_25_n47# and_cla_0/gnd Gnd nfet w=12
l=4
+ ad=768 pd=200 as=0 ps=0
M1010 xor_cla_1/a_n40_n43# xor_cla_1/a_n22_n46# xor_cla_1/a_n40_19#
xor_cla_1/w_n72_13# pfet w=19 l=4
+ ad=380 pd=78 as=342 ps=74
M1011 xor_cla_1/a_n40_19# xor_cla_1/a_n49_n11# and_cla_0/vdd
xor_cla_1/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1012 xor_cla_1/a_6_19# xor_cla_1/a_2_n49# xor_cla_1/a_n40_n43#
xor_cla_1/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1013 xor_cla_1/a_n61_n43# xor_cla_1/a_n22_n46# xor_cla_1/a_n40_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=216 ps=60
M1014 and_cla_0/gnd xor_cla_1/a_2_n49# xor_cla_1/a_n61_n43# Gnd nfet w=12
l=4
+ ad=0 pd=0 as=0 ps=0
M1015 xor_cla_1/a_n40_n43# xor_cla_1/a_n49_n11# xor_cla_1/a_n61_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=0 ps=0
M1016 and_cla_0/vdd xor_cla_2/a_25_n47# xor_cla_2/a_6_19#
xor_cla_2/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=361 ps=76
M1017 xor_cla_2/a_n61_n43# xor_cla_2/a_25_n47# and_cla_0/gnd Gnd nfet w=12
l=4
+ ad=768 pd=200 as=0 ps=0
M1018 xor_cla_2/a_n40_n43# xor_cla_2/a_n22_n46# xor_cla_2/a_n40_19#
xor_cla_2/w_n72_13# pfet w=19 l=4
+ ad=380 pd=78 as=342 ps=74
M1019 xor_cla_2/a_n40_19# xor_cla_2/a_n49_n11# and_cla_0/vdd
xor_cla_2/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1020 xor_cla_2/a_6_19# xor_cla_2/a_2_n49# xor_cla_2/a_n40_n43#
xor_cla_2/w_n72_13# pfet w=19 l=4

```



```

+ ad=0 pd=0 as=0 ps=0
M1021 xor_cla_2/a_n61_n43# xor_cla_2/a_n22_n46# xor_cla_2/a_n40_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=216 ps=60
M1022 and_cla_0/gnd xor_cla_2/a_2_n49# xor_cla_2/a_n61_n43# Gnd nfet w=12
l=4
+ ad=0 pd=0 as=0 ps=0
M1023 xor_cla_2/a_n40_n43# xor_cla_2/a_n49_n11# xor_cla_2/a_n61_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=0 ps=0
M1024 and_cla_0/vdd xor_cla_3/a_25_n47# xor_cla_3/a_6_19#
xor_cla_3/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=361 ps=76
M1025 xor_cla_3/a_n61_n43# xor_cla_3/a_25_n47# and_cla_0/gnd Gnd nfet w=12
l=4
+ ad=768 pd=200 as=0 ps=0
M1026 xor_cla_3/a_n40_n43# xor_cla_3/a_n22_n46# xor_cla_3/a_n40_19#
xor_cla_3/w_n72_13# pfet w=19 l=4
+ ad=380 pd=78 as=342 ps=74
M1027 xor_cla_3/a_n40_19# m1_n356_79# and_cla_0/vdd xor_cla_3/w_n72_13#
pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1028 xor_cla_3/a_6_19# xor_cla_3/a_2_n49# xor_cla_3/a_n40_n43#
xor_cla_3/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1029 xor_cla_3/a_n61_n43# xor_cla_3/a_n22_n46# xor_cla_3/a_n40_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=216 ps=60
M1030 and_cla_0/gnd xor_cla_3/a_2_n49# xor_cla_3/a_n61_n43# Gnd nfet w=12
l=4
+ ad=0 pd=0 as=0 ps=0
M1031 xor_cla_3/a_n40_n43# m1_n356_79# xor_cla_3/a_n61_n43# Gnd nfet w=12
l=4
+ ad=0 pd=0 as=0 ps=0
M1032 and_cla_0/gnd and_cla_0/a_n23_18# and_cla_0/vdd and_cla_0/w_37_6#
pfet w=10 l=4
+ ad=1080 pd=296 as=0 ps=0
M1033 and_cla_0/a_n23_18# and_cla_0/a_n9_n16# and_cla_0/a_n23_n34# Gnd
nfet w=8 l=4
+ ad=72 pd=34 as=136 ps=50

```



```

M1034 and_cla_0/a_n23_18# and_cla_0/a_n30_n14# and_cla_0/vdd
and_cla_0/w_n44_12# pfet w=10 l=4
+ ad=170 pd=54 as=0 ps=0
** SOURCE/DRAIN TIED
M1035 and_cla_0/gnd and_cla_0/a_n23_18# and_cla_0/gnd Gnd nfet w=9 l=4
+ ad=0 pd=0 as=0 ps=0
M1036 and_cla_0/vdd and_cla_0/a_n9_n16# and_cla_0/a_n23_18#
and_cla_0/w_n44_12# pfet w=10 l=4
+ ad=0 pd=0 as=0 ps=0
M1037 and_cla_0/a_n23_n34# and_cla_0/a_n30_n14# and_cla_0/gnd Gnd nfet w=8
l=4
+ ad=0 pd=0 as=0 ps=0
M1038 and_cla_0/gnd and_cla_1/a_n23_18# and_cla_0/vdd and_cla_1/w_37_6#
pfet w=10 l=4
+ ad=0 pd=0 as=0 ps=0
M1039 and_cla_1/a_n23_18# and_cla_1/a_n9_n16# and_cla_1/a_n23_n34# Gnd
nfet w=8 l=4
+ ad=72 pd=34 as=136 ps=50
M1040 and_cla_1/a_n23_18# and_cla_1/a_n30_n14# and_cla_0/vdd
and_cla_1/w_n44_12# pfet w=10 l=4
+ ad=170 pd=54 as=0 ps=0
** SOURCE/DRAIN TIED
M1041 and_cla_0/gnd and_cla_1/a_n23_18# and_cla_0/gnd Gnd nfet w=9 l=4
+ ad=0 pd=0 as=0 ps=0
M1042 and_cla_0/vdd and_cla_1/a_n9_n16# and_cla_1/a_n23_18#
and_cla_1/w_n44_12# pfet w=10 l=4
+ ad=0 pd=0 as=0 ps=0
M1043 and_cla_1/a_n23_n34# and_cla_1/a_n30_n14# and_cla_0/gnd Gnd nfet w=8
l=4
+ ad=0 pd=0 as=0 ps=0
M1044 and_cla_0/gnd and_cla_3/a_n23_18# and_cla_0/vdd and_cla_3/w_37_6#
pfet w=10 l=4
+ ad=0 pd=0 as=0 ps=0
M1045 and_cla_3/a_n23_18# and_cla_3/a_n9_n16# and_cla_3/a_n23_n34# Gnd
nfet w=8 l=4
+ ad=72 pd=34 as=136 ps=50
M1046 and_cla_3/a_n23_18# and_cla_3/a_n30_n14# and_cla_0/vdd
and_cla_3/w_n44_12# pfet w=10 l=4
+ ad=170 pd=54 as=0 ps=0
** SOURCE/DRAIN TIED


```

```

M1047 and_cla_0/gnd and_cla_3/a_n23_18# and_cla_0/gnd Gnd nfet w=9 l=4
+ ad=0 pd=0 as=0 ps=0
M1048 and_cla_0/vdd and_cla_3/a_n9_n16# and_cla_3/a_n23_18#
and_cla_3/w_n44_12# pfet w=10 l=4
+ ad=0 pd=0 as=0 ps=0
M1049 and_cla_3/a_n23_n34# and_cla_3/a_n30_n14# and_cla_0/gnd Gnd nfet w=8
l=4
+ ad=0 pd=0 as=0 ps=0
M1050 and_cla_0/gnd and_cla_2/a_n23_18# and_cla_0/vdd and_cla_2/w_37_6#
pfet w=10 l=4
+ ad=0 pd=0 as=0 ps=0
M1051 and_cla_2/a_n23_18# and_cla_2/a_n9_n16# and_cla_2/a_n23_n34# Gnd
nfet w=8 l=4
+ ad=72 pd=34 as=136 ps=50
M1052 and_cla_2/a_n23_18# and_cla_2/a_n30_n14# and_cla_0/vdd
and_cla_2/w_n44_12# pfet w=10 l=4
+ ad=170 pd=54 as=0 ps=0
** SOURCE/DRAIN TIED
M1053 and_cla_0/gnd and_cla_2/a_n23_18# and_cla_0/gnd Gnd nfet w=9 l=4
+ ad=0 pd=0 as=0 ps=0
M1054 and_cla_0/vdd and_cla_2/a_n9_n16# and_cla_2/a_n23_18#
and_cla_2/w_n44_12# pfet w=10 l=4
+ ad=0 pd=0 as=0 ps=0
M1055 and_cla_2/a_n23_n34# and_cla_2/a_n30_n14# and_cla_0/gnd Gnd nfet w=8
l=4
+ ad=0 pd=0 as=0 ps=0

* Output
.control
tran 1n 200n
run
plot v(p1) v(g1)
plot v(p2) v(g2)
plot v(p3) v(g3)
plot v(p4) v(g4)
set curplottitle= "Srujana Vanka - 2020102005 - PGblock"
.endc
.end

```

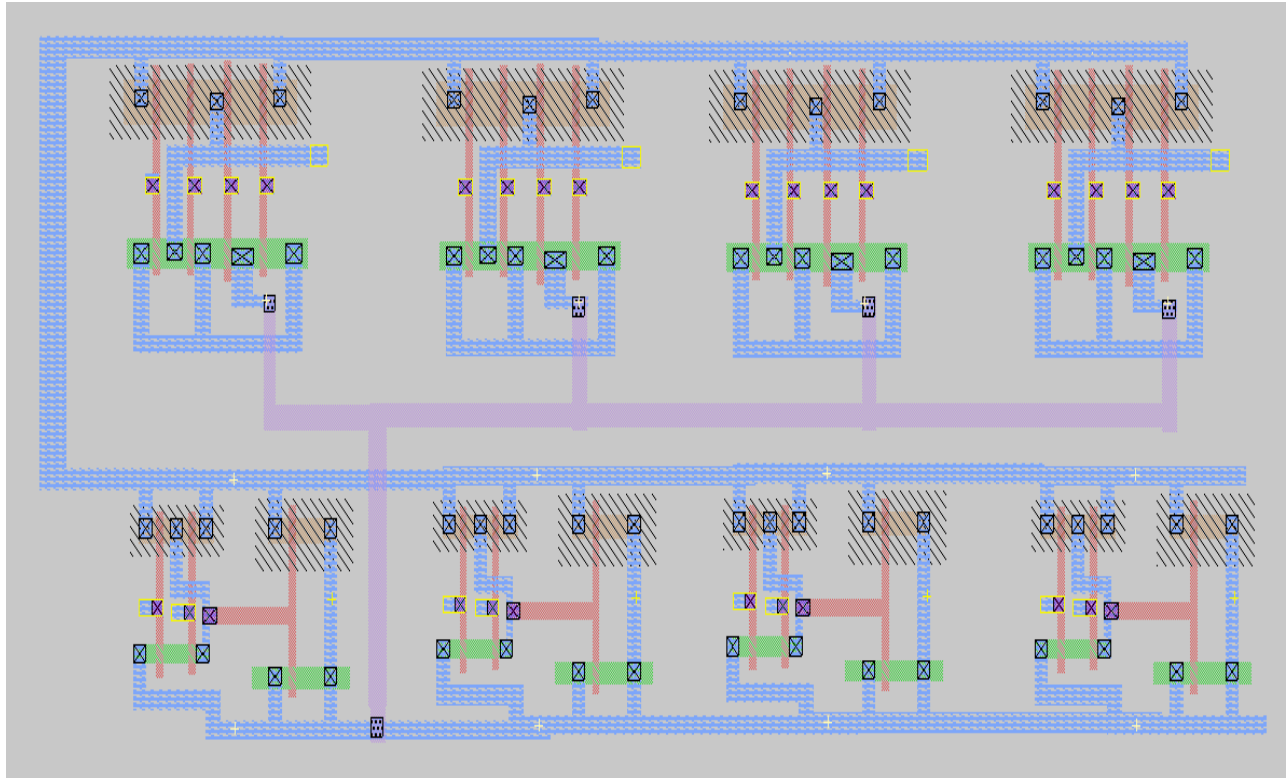

Carry block

```
* SPICE3 file created from carry.ext - technology: scmos
*Carry look ahead block*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param w = {10*LAMBDA}
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'
.option scale=0.09u

M1000 a_507_77# g1 nand_0/vdd nand_0/w_n39_n8# CMOSP w=14 l=3
+ ad=336 pd=104 as=350 ps=106
M1001 a_507_77# g2 nand_0/vdd nand_0/w_n39_n8# CMOSP w=14 l=3
+ ad=0 pd=0 as=0 ps=0
```

```
M1002 nand_0/vdd p2 a_507_77# nand_0/w_n39_n8# CMOSP w=14 l=3
+ ad=0 pd=0 as=0 ps=0
M1003 nand_0/a_n18_n51# g2 nand_0/gnd Gnd CMOSN w=9 l=3
+ ad=108 pd=42 as=180 ps=58
M1004 nand_0/a_n3_n51# p2 nand_0/a_n18_n51# Gnd CMOSN w=9 l=3
+ ad=135 pd=48 as=0 ps=0
M1005 a_507_77# g1 nand_0/a_n3_n51# Gnd CMOSN w=9 l=3
+ ad=243 pd=72 as=0 ps=0
M1006 nor3_0/not_cla_0/a_3_n37# a_681_n2# nor3_0/not_cla_0/vdd
nor3_0/not_cla_0/w_n20_n1# CMOSP w=9 l=3
+ ad=135 pd=48 as=117 ps=44
M1007 nor3_0/not_cla_0/a_3_n37# a_681_n2# nor3_0/not_cla_0/gnd Gnd CMOSN
w=9 l=3
+ ad=225 pd=68 as=198 ps=62
M1008 a_681_n2# a_591_67# nor3_0/gnd Gnd CMOSN w=8 l=3
+ ad=320 pd=112 as=192 ps=80
M1009 nor3_0/gnd a_605_63# a_681_n2# Gnd CMOSN w=8 l=3
+ ad=0 pd=0 as=0 ps=0
M1010 a_681_n2# and_cla_1/gnd nor3_0/a_n7_n5# nor3_0/w_n39_n12# CMOSP w=9
l=3
+ ad=99 pd=40 as=108 ps=42
M1011 nor3_0/a_n7_n5# a_605_63# nor3_0/a_n21_n5# nor3_0/w_n39_n12# CMOSP
w=9 l=3
+ ad=0 pd=0 as=99 ps=40
M1012 nor3_0/a_n21_n5# a_591_67# nor3_0/vdd nor3_0/w_n39_n12# CMOSP w=9
l=3
+ ad=0 pd=0 as=81 ps=36
M1013 a_681_n2# and_cla_1/gnd nor3_0/gnd Gnd CMOSN w=8 l=3
+ ad=0 pd=0 as=0 ps=0
M1014 p4p3g2 a_312_n209# nor3_1/not_cla_0/vdd nor3_1/not_cla_0/w_n20_n1#
CMOSP w=9 l=3
+ ad=135 pd=48 as=117 ps=44
M1015 p4p3g2 a_312_n209# nor3_1/not_cla_0/gnd Gnd CMOSN w=9 l=3
+ ad=225 pd=68 as=198 ps=62
M1016 a_312_n209# g2 nor3_1/gnd Gnd CMOSN w=8 l=3
+ ad=320 pd=112 as=192 ps=80
M1017 nor3_1/gnd g2 a_312_n209# Gnd CMOSN w=8 l=3
+ ad=0 pd=0 as=0 ps=0
M1018 a_312_n209# a_256_n157# nor3_1/a_n7_n5# nor3_1/w_n39_n12# CMOSP w=9
l=3
```

```

+ ad=99 pd=40 as=108 ps=42
M1019 nor3_1/a_n7_n5# g2 nor3_1/a_n21_n5# nor3_1/w_n39_n12# CMOSP w=9 l=3
+ ad=0 pd=0 as=99 ps=40
M1020 nor3_1/a_n21_n5# g2 nor3_1/vdd nor3_1/w_n39_n12# CMOSP w=9 l=3
+ ad=0 pd=0 as=81 ps=36
M1021 a_312_n209# a_256_n157# nor3_1/gnd Gnd CMOSN w=8 l=3
+ ad=0 pd=0 as=0 ps=0
M1022 p4p3p2g1 a_418_n113# and4_0/not_cla_0/vdd and4_0/not_cla_0/w_n20_n1#
CMOSP w=9 l=3
+ ad=135 pd=48 as=117 ps=44
M1023 p4p3p2g1 a_418_n113# and4_0/not_cla_0/gnd Gnd CMOSN w=9 l=3
+ ad=225 pd=68 as=198 ps=62
M1024 a_418_n113# g1 and4_0/a_16_n59# Gnd CMOSN w=13 l=3
+ ad=325 pd=76 as=364 ps=82
M1025 and4_0/a_n41_n59# g2 and4_0/gnd Gnd CMOSN w=13 l=3
+ ad=299 pd=72 as=286 ps=70
M1026 and4_0/vdd g1 a_418_n113# and4_0/w_n67_17# CMOSP w=11 l=3
+ ad=616 pd=178 as=561 ps=146
M1027 and4_0/a_16_n59# p2 and4_0/a_n15_n59# Gnd CMOSN w=13 l=3
+ ad=0 pd=0 as=364 ps=82
M1028 a_418_n113# g2 and4_0/vdd and4_0/w_n67_17# CMOSP w=11 l=3
+ ad=0 pd=0 as=0 ps=0
M1029 a_418_n113# p2 and4_0/vdd and4_0/w_n67_17# CMOSP w=11 l=3
+ ad=0 pd=0 as=0 ps=0
M1030 and4_0/vdd g2 a_418_n113# and4_0/w_n67_17# CMOSP w=11 l=3
+ ad=0 pd=0 as=0 ps=0
M1031 and4_0/a_n15_n59# g2 and4_0/a_n41_n59# Gnd CMOSN w=13 l=3
+ ad=0 pd=0 as=0 ps=0
M1032 cout or4_0/gnd or4_0/not_cla_0/vdd or4_0/not_cla_0/w_n20_n1# CMOSP
w=9 l=3
+ ad=135 pd=48 as=117 ps=44
M1033 cout or4_0/gnd or4_0/not_cla_0/gnd Gnd CMOSN w=9 l=3
+ ad=225 pd=68 as=198 ps=62
M1034 or4_0/a_n5_9# or4_0/a_n8_n59# or4_0/a_n21_9# or4_0/w_n42_0# CMOSP
w=12 l=3
+ ad=156 pd=50 as=156 ps=50
M1035 or4_0/gnd g4 or4_0/a_11_n56# Gnd CMOSN w=8 l=3
+ ad=352 pd=136 as=96 ps=40
M1036 or4_0/a_11_9# or4_0/a_8_n60# or4_0/a_n5_9# or4_0/w_n42_0# CMOSP w=12
l=3

```

```

+ ad=144 pd=48 as=0 ps=0
M1037 or4_0/gnd or4_0/a_n8_n59# or4_0/a_n21_n56# Gnd CMOSN w=8 l=3
+ ad=0 pd=0 as=104 ps=42
M1038 or4_0/a_n21_n56# or4_0/a_n24_n59# or4_0/gnd Gnd CMOSN w=8 l=3
+ ad=0 pd=0 as=0 ps=0
M1039 or4_0/a_n21_9# or4_0/a_n24_n59# or4_0/vdd or4_0/w_n42_0# CMOSP w=12
l=3
+ ad=0 pd=0 as=120 ps=44
M1040 or4_0/gnd g4 or4_0/a_11_9# or4_0/w_n42_0# CMOSP w=12 l=3
+ ad=120 pd=44 as=0 ps=0
M1041 or4_0/a_11_n56# or4_0/a_8_n60# or4_0/gnd Gnd CMOSN w=8 l=3
+ ad=0 pd=0 as=0 ps=0
M1042 a_591_67# a_507_77# not_cla_0/vdd not_cla_0/w_n20_n1# CMOSP w=9 l=3
+ ad=135 pd=48 as=117 ps=44
M1043 a_591_67# a_507_77# not_cla_0/gnd Gnd CMOSN w=9 l=3
+ ad=225 pd=68 as=198 ps=62
M1044 p2g1 and_cla_0/a_n23_18# and_cla_0/vdd and_cla_0/w_37_6# CMOSP w=10
l=4
+ ad=270 pd=74 as=360 ps=132
M1045 and_cla_0/a_n23_18# m1_n11_79# and_cla_0/a_n23_n34# Gnd CMOSN w=8
l=4
+ ad=72 pd=34 as=136 ps=50
M1046 and_cla_0/a_n23_18# p1 and_cla_0/vdd and_cla_0/w_n44_12# CMOSP w=10
l=4
+ ad=170 pd=54 as=0 ps=0
** SOURCE/DRAIN TIED
M1047 p2g1 and_cla_0/a_n23_18# p2g1 Gnd CMOSN w=9 l=4
+ ad=651 pd=200 as=0 ps=0
M1048 and_cla_0/vdd m1_n11_79# and_cla_0/a_n23_18# and_cla_0/w_n44_12#
CMOSP w=10 l=4
+ ad=0 pd=0 as=0 ps=0
M1049 and_cla_0/a_n23_n34# p1 p2g1 Gnd CMOSN w=8 l=4
+ ad=0 pd=0 as=0 ps=0
M1050 and_cla_1/gnd and_cla_1/a_n23_18# and_cla_1/vdd and_cla_1/w_37_6#
CMOSP w=10 l=4
+ ad=270 pd=74 as=360 ps=132
M1051 and_cla_1/a_n23_18# g2 and_cla_1/a_n23_n34# Gnd CMOSN w=8 l=4
+ ad=72 pd=34 as=136 ps=50
M1052 and_cla_1/a_n23_18# g2 and_cla_1/vdd and_cla_1/w_n44_12# CMOSP w=10
l=4

```

```

+ ad=170 pd=54 as=0 ps=0
** SOURCE/DRAIN TIED
M1053 and_cla_1/gnd and_cla_1/a_n23_18# and_cla_1/gnd Gnd CMOSN w=9 l=4
+ ad=651 pd=200 as=0 ps=0
M1054 and_cla_1/vdd g2 and_cla_1/a_n23_18# and_cla_1/w_n44_12# CMOSP w=10
l=4
+ ad=0 pd=0 as=0 ps=0
M1055 and_cla_1/a_n23_n34# g2 and_cla_1/gnd Gnd CMOSN w=8 l=4
+ ad=0 pd=0 as=0 ps=0
M1056 p4g3 and_cla_2/a_n23_18# and_cla_2/vdd and_cla_2/w_37_6# CMOSP w=10
l=4
+ ad=270 pd=74 as=360 ps=132
M1057 and_cla_2/a_n23_18# m1_272_n368# and_cla_2/a_n23_n34# Gnd CMOSN w=8
l=4
+ ad=72 pd=34 as=136 ps=50
M1058 and_cla_2/a_n23_18# m1_250_n366# and_cla_2/vdd and_cla_2/w_n44_12#
CMOSP w=10 l=4
+ ad=170 pd=54 as=0 ps=0
** SOURCE/DRAIN TIED
M1059 p4g3 and_cla_2/a_n23_18# p4g3 Gnd CMOSN w=9 l=4
+ ad=651 pd=200 as=0 ps=0
M1060 and_cla_2/vdd m1_272_n368# and_cla_2/a_n23_18# and_cla_2/w_n44_12#
CMOSP w=10 l=4
+ ad=0 pd=0 as=0 ps=0
M1061 and_cla_2/a_n23_n34# m1_250_n366# p4g3 Gnd CMOSN w=8 l=4
+ ad=0 pd=0 as=0 ps=0
M1062 or_cla_0/a_74_n55# or_cla_0/a_n6_n54# or_cla_0/gnd Gnd CMOSN w=16
l=3
+ ad=464 pd=90 as=1056 ps=228
M1063 or_cla_0/a_n6_n54# m1_154_106# or_cla_0/a_n6_14# or_cla_0/w_n27_6#
CMOSP w=9 l=3
+ ad=144 pd=50 as=117 ps=44
M1064 or_cla_0/a_n6_n54# p2g1 or_cla_0/gnd Gnd CMOSN w=16 l=3
+ ad=208 pd=58 as=0 ps=0
M1065 or_cla_0/gnd m1_154_106# or_cla_0/a_n6_n54# Gnd CMOSN w=16 l=3
+ ad=0 pd=0 as=0 ps=0
M1066 or_cla_0/a_n6_14# p2g1 or_cla_0/vdd or_cla_0/w_n27_6# CMOSP w=9 l=3
+ ad=0 pd=0 as=324 ps=108
M1067 or_cla_0/a_74_n55# or_cla_0/a_n6_n54# or_cla_0/vdd or_cla_0/w_41_7#
CMOSP w=9 l=3

```

```
+ ad=243 pd=72 as=0 ps=0
C0 or4_0/a_11_n56# or4_0/gnd 0.12fF
C1 m1_250_n366# p1 0.03fF
C2 and_cla_1/a_n23_18# and_cla_1/w_n44_12# 0.04fF
C3 nor3_1/vdd nor3_1/w_n39_n12# 0.17fF
C4 m1_272_n368# g1 0.03fF
C5 a_418_n113# g1 0.16fF
C6 and_cla_2/a_n23_18# and_cla_2/w_37_6# 0.16fF
C7 and_cla_2/vdd and_cla_2/w_n44_12# 0.06fF
C8 a_681_n2# nor3_0/not_cla_0/w_n20_n1# 0.09fF
C9 g3 g4 0.36fF
C10 g2 nor3_1/w_n39_n12# 0.25fF
C11 or_cla_0/a_74_n55# g2 0.08fF
C12 a_591_67# nor3_0/w_n39_n12# 0.13fF
C13 or4_0/gnd cout 0.10fF
C14 and4_0/not_cla_0/vdd p4p3p2g1 0.06fF
C15 or_cla_0/a_n6_n54# or_cla_0/w_41_7# 0.11fF
C16 or_cla_0/vdd or_cla_0/w_n27_6# 0.03fF
C17 nor3_1/not_cla_0/vdd a_312_n209# 0.08fF
C18 p4p3g2 nor3_1/not_cla_0/w_n20_n1# 0.05fF
C19 m3_256_n157# p2 0.11fF
C20 p1 g1 4.67fF
C21 or4_0/a_n21_n56# or4_0/gnd 0.05fF
C22 g4 g1 0.34fF
C23 a_256_n157# nor3_1/w_n39_n12# 0.13fF
C24 m1_272_n368# p2 0.03fF
C25 a_418_n113# p2 0.16fF
C26 or4_0/a_n24_n59# or4_0/w_n42_0# 0.13fF
C27 p1 and_cla_0/w_n44_12# 0.09fF
C28 and_cla_2/a_n23_n34# m1_272_n368# 0.01fF
C29 nor3_0/vdd a_681_n2# 0.07fF
C30 and4_0/not_cla_0/gnd p4p3p2g1 0.09fF
C31 or4_0/gnd or4_0/not_cla_0/vdd 0.08fF
C32 g3 m1_250_n366# 0.03fF
C33 or_cla_0/a_n6_n54# or_cla_0/w_n27_6# 0.04fF
C34 m1_154_106# p2g1 0.05fF
C35 nor3_1/not_cla_0/vdd nor3_1/not_cla_0/w_n20_n1# 0.08fF
C36 p1 p2 0.60fF
C37 g4 p2 0.36fF
C38 p4p3p2g1 and4_0/not_cla_0/w_n20_n1# 0.05fF
```



```
C39 g2 and_cla_1/w_n44_12# 0.18fF
C40 or4_0/a_n24_n59# p4p3p2g1 0.16fF
C41 or4_0/a_n8_n59# p4p3g2 0.16fF
C42 a_507_77# nand_0/gnd 0.05fF
C43 m1_272_n368# g2 0.06fF
C44 nand_0/vdd g1 0.13fF
C45 g2 a_418_n113# 0.16fF
C46 m3_256_n157# a_256_n157# 0.08fF
C47 m1_250_n366# g1 0.03fF
C48 not_cla_0/vdd a_591_67# 0.06fF
C49 and_cla_2/a_n23_18# and_cla_2/w_n44_12# 0.04fF
C50 p4 g4 5.22fF
C51 p4g3 m1_272_n368# 0.40fF
C52 and4_0/w_n67_17# a_418_n113# 0.12fF
C53 and_cla_0/a_n23_18# m1_n11_79# 0.44fF
C54 and4_0/not_cla_0/vdd a_418_n113# 0.08fF
C55 p4g3 p4p3g2 0.54fF
C56 g2 p1 1.10fF
C57 a_312_n209# nor3_1/not_cla_0/w_n20_n1# 0.09fF
C58 g2 g4 0.72fF
C59 nand_0/vdd p2 0.13fF
C60 p4g3 or4_0/a_n21_n56# 0.09fF
C61 m1_250_n366# p2 0.03fF
C62 cout or4_0/not_cla_0/w_n20_n1# 0.05fF
C63 and_cla_1/gnd a_681_n2# 0.13fF
C64 a_507_77# a_591_67# 0.03fF
C65 m1_272_n368# and_cla_2/w_n44_12# 0.09fF
C66 a_605_63# a_681_n2# 0.13fF
C67 and4_0/not_cla_0/gnd a_418_n113# 0.05fF
C68 and_cla_0/vdd and_cla_0/w_37_6# 0.05fF
C69 p4 m1_250_n366# 0.20fF
C70 a_418_n113# and4_0/not_cla_0/w_n20_n1# 0.09fF
C71 or_cla_0/a_n6_14# m1_154_106# 0.01fF
C72 nor3_1/vdd a_312_n209# 0.07fF
C73 g2 nand_0/vdd 0.13fF
C74 or4_0/a_n24_n59# p4p3g2 0.16fF
C75 a_507_77# nand_0/vdd 0.11fF
C76 m1_250_n366# g2 1.69fF
C77 g1 p2 0.60fF
C78 m1_154_106# p1 0.02fF
```

C79 g3 p4 3.47fF
C80 or4_0/not_cla_0/vdd or4_0/not_cla_0/w_n20_n1# 0.08fF
C81 g2 a_312_n209# 0.13fF
C82 nor3_0/not_cla_0/gnd nor3_0/not_cla_0/a_3_n37# 0.09fF
C83 or4_0/vdd or4_0/w_n42_0# 0.05fF
C84 g3 g2 3.47fF
C85 m1_154_106# or_cla_0/w_n27_6# 0.28fF
C86 a_256_n157# a_312_n209# 0.13fF
C87 m3_256_n157# p4p3p2g1 0.22fF
C88 and_cla_1/a_n23_18# g2 0.46fF
C89 and_cla_1/gnd and_cla_1/w_37_6# 0.07fF
C90 p4g3 or4_0/a_8_n60# 0.10fF
C91 g2 g1 1.21fF
C92 a_507_77# g1 0.09fF
C93 nand_0/vdd nand_0/w_n39_n8# 0.27fF
C94 p4g3 or4_0/gnd 0.19fF
C95 not_cla_0/w_n20_n1# a_591_67# 0.05fF
C96 m1_250_n366# and_cla_2/w_n44_12# 0.09fF
C97 and_cla_1/gnd nor3_0/vdd 0.09fF
C98 and4_0/w_n67_17# g1 0.14fF
C99 nor3_0/w_n39_n12# a_681_n2# 0.04fF
C100 m1_272_n368# p4p3p2g1 0.19fF
C101 g2 and4_0/gnd 0.18fF
C102 p4p3p2g1 a_418_n113# 0.07fF
C103 g4 or4_0/w_n42_0# 0.13fF
C104 or4_0/gnd or4_0/not_cla_0/w_n20_n1# 0.09fF
C105 and_cla_0/a_n23_18# and_cla_0/w_37_6# 0.16fF
C106 and_cla_0/vdd and_cla_0/w_n44_12# 0.06fF
C107 nor3_0/vdd a_605_63# 0.09fF
C108 p4p3p2g1 p4p3g2 1.19fF
C109 or_cla_0/vdd m1_154_106# 0.13fF
C110 or_cla_0/a_74_n55# or_cla_0/w_41_7# 0.03fF
C111 and4_0/gnd a_256_n157# 0.15fF
C112 and_cla_1/vdd and_cla_1/w_37_6# 0.05fF
C113 g2 p2 4.69fF
C114 not_cla_0/vdd a_507_77# 0.08fF
C115 a_507_77# p2 0.09fF
C116 g1 nand_0/w_n39_n8# 0.15fF
C117 and4_0/w_n67_17# p2 0.14fF
C118 and_cla_2/a_n23_18# m1_272_n368# 0.46fF

C119 p4g3 and_cla_2/w_37_6# 0.07fF
C120 nor3_0/not_cla_0/a_3_n37# nor3_0/not_cla_0/vdd 0.06fF
C121 m1_154_106# g1 0.14fF
C122 g2 nor3_1/vdd 0.44fF
C123 and4_0/vdd g1 0.23fF
C124 m1_n11_79# p1 0.96fF
C125 nor3_0/vdd a_591_67# 0.09fF
C126 p2g1 or_cla_0/w_n27_6# 0.11fF
C127 or_cla_0/a_n6_n54# m1_154_106# 0.28fF
C128 nor3_1/not_cla_0/gnd p4p3g2 0.09fF
C129 nor3_1/vdd a_256_n157# 0.17fF
C130 p4g3 or4_0/a_n8_n59# 0.16fF
C131 p2g1 and_cla_0/w_37_6# 0.07fF
C132 p2 nand_0/w_n39_n8# 0.15fF
C133 m1_272_n368# and_cla_1/gnd 0.16fF
C134 g2 and4_0/w_n67_17# 0.28fF
C135 or4_0/not_cla_0/gnd cout 0.09fF
C136 nor3_0/not_cla_0/a_3_n37# a_681_n2# 0.09fF
C137 m1_272_n368# a_605_63# 0.05fF
C138 or4_0/a_8_n60# or4_0/w_n42_0# 0.13fF
C139 and4_0/vdd p2 0.28fF
C140 and_cla_0/a_n23_18# and_cla_0/w_n44_12# 0.04fF
C141 nor3_0/vdd nor3_0/w_n39_n12# 0.17fF
C142 nor3_0/gnd a_681_n2# 0.16fF
C143 m1_272_n368# p4p3g2 0.19fF
C144 or4_0/gnd or4_0/w_n42_0# 0.06fF
C145 nor3_1/w_n39_n12# a_312_n209# 0.04fF
C146 m1_272_n368# p1 0.03fF
C147 and_cla_1/a_n23_18# and_cla_1/w_37_6# 0.16fF
C148 and_cla_1/vdd and_cla_1/w_n44_12# 0.06fF
C149 g2 nand_0/w_n39_n8# 0.15fF
C150 not_cla_0/vdd not_cla_0/w_n20_n1# 0.08fF
C151 a_507_77# nand_0/w_n39_n8# 0.10fF
C152 not_cla_0/gnd a_591_67# 0.09fF
C153 and_cla_2/vdd and_cla_2/w_37_6# 0.05fF
C154 nor3_0/not_cla_0/vdd a_681_n2# 0.08fF
C155 nor3_0/not_cla_0/a_3_n37# nor3_0/not_cla_0/w_n20_n1# 0.05fF
C156 g2 and4_0/vdd 0.88fF
C157 p1 g4 0.34fF
C158 and4_0/vdd and4_0/w_n67_17# 0.13fF


```
C159 p4p3g2 nor3_1/not_cla_0/vdd 0.06fF
C160 m1_n11_79# g1 0.31fF
C161 nor3_1/gnd a_312_n209# 0.16fF
C162 p4g3 or4_0/a_n24_n59# 0.16fF
C163 a_507_77# not_cla_0/w_n20_n1# 0.09fF
C164 and4_0/not_cla_0/vdd and4_0/not_cla_0/w_n20_n1# 0.08fF
C165 cout or4_0/not_cla_0/vdd 0.06fF
C166 and_cla_1/gnd nor3_0/w_n39_n12# 0.13fF
C167 m1_272_n368# m1_250_n366# 0.04fF
C168 nor3_0/not_cla_0/vdd nor3_0/not_cla_0/w_n20_n1# 0.08fF
C169 or4_0/a_n8_n59# or4_0/w_n42_0# 0.13fF
C170 m1_n11_79# and_cla_0/w_n44_12# 0.09fF
C171 a_605_63# nor3_0/w_n39_n12# 0.13fF
C172 g3 m1_272_n368# 0.20fF
C173 p4p3g2 a_312_n209# 0.05fF
C174 or_cla_0/vdd or_cla_0/w_41_7# 0.03fF
C175 m3_256_n157# g1 0.13fF
C176 g3 Gnd 17.85fF **FLOATING
C177 p4 Gnd 17.86fF **FLOATING
C178 or_cla_0/gnd Gnd 0.71fF
C179 or_cla_0/a_74_n55# Gnd 0.31fF
C180 or_cla_0/vdd Gnd 0.46fF
C181 or_cla_0/a_n6_n54# Gnd 1.17fF
C182 p2g1 Gnd 1.79fF
C183 or_cla_0/w_41_7# Gnd 1.55fF
C184 or_cla_0/w_n27_6# Gnd 1.42fF
C185 p4g3 Gnd 1.67fF
C186 and_cla_2/vdd Gnd 0.68fF
C187 and_cla_2/a_n23_18# Gnd 1.14fF
C188 m1_272_n368# Gnd 1.48fF
C189 m1_250_n366# Gnd 0.74fF
C190 and_cla_2/w_37_6# Gnd 1.96fF
C191 and_cla_2/w_n44_12# Gnd 1.33fF
C192 and_cla_1/gnd Gnd 1.68fF
C193 and_cla_1/vdd Gnd 0.68fF
C194 and_cla_1/a_n23_18# Gnd 1.14fF
C195 g2 Gnd 45.57fF
C196 and_cla_1/w_37_6# Gnd 1.96fF
C197 and_cla_1/w_n44_12# Gnd 1.33fF
C198 and_cla_0/vdd Gnd 0.68fF
```

C199 and_cla_0/a_n23_18# Gnd 1.14fF
C200 m1_n11_79# Gnd 1.07fF
C201 p1 Gnd 19.76fF
C202 and_cla_0/w_37_6# Gnd 1.96fF
C203 and_cla_0/w_n44_12# Gnd 1.33fF
C204 not_cla_0/gnd Gnd 0.20fF
C205 not_cla_0/vdd Gnd 0.12fF
C206 a_507_77# Gnd 0.53fF
C207 not_cla_0/w_n20_n1# Gnd 0.93fF
C208 or4_0/a_11_n56# Gnd 0.02fF
C209 or4_0/a_n21_n56# Gnd 0.02fF
C210 or4_0/gnd Gnd 1.60fF
C211 or4_0/vdd Gnd 0.41fF
C212 g4 Gnd 20.54fF
C213 or4_0/a_8_n60# Gnd 0.40fF
C214 or4_0/a_n8_n59# Gnd 0.39fF
C215 or4_0/a_n24_n59# Gnd 0.38fF
C216 or4_0/w_n42_0# Gnd 2.45fF
C217 or4_0/not_cla_0/gnd Gnd 0.20fF
C218 cout Gnd 0.18fF
C219 or4_0/not_cla_0/vdd Gnd 0.12fF
C220 or4_0/not_cla_0/w_n20_n1# Gnd 0.93fF
C221 and4_0/gnd Gnd 0.60fF
C222 and4_0/vdd Gnd 0.65fF
C223 and4_0/w_n67_17# Gnd 4.31fF
C224 and4_0/not_cla_0/gnd Gnd 0.20fF
C225 p4p3p2g1 Gnd 0.37fF
C226 and4_0/not_cla_0/vdd Gnd 0.12fF
C227 a_418_n113# Gnd 1.62fF
C228 and4_0/not_cla_0/w_n20_n1# Gnd 0.93fF
C229 nor3_1/gnd Gnd 0.39fF
C230 nor3_1/vdd Gnd 0.00fF
C231 a_256_n157# Gnd 0.34fF
C232 nor3_1/w_n39_n12# Gnd 1.70fF
C233 nor3_1/not_cla_0/gnd Gnd 0.20fF
C234 p4p3g2 Gnd 0.39fF
C235 nor3_1/not_cla_0/vdd Gnd 0.12fF
C236 a_312_n209# Gnd 0.90fF
C237 nor3_1/not_cla_0/w_n20_n1# Gnd 0.93fF
C238 nor3_0/gnd Gnd 0.39fF

```
C239 nor3_0/vdd Gnd 0.00fF
C240 a_605_63# Gnd 0.34fF
C241 a_591_67# Gnd 0.57fF
C242 nor3_0/w_n39_n12# Gnd 1.70fF
C243 nor3_0/not_cla_0/gnd Gnd 0.20fF
C244 nor3_0/not_cla_0/a_3_n37# Gnd 0.14fF
C245 nor3_0/not_cla_0/vdd Gnd 0.12fF
C246 a_681_n2# Gnd 0.97fF
C247 nor3_0/not_cla_0/w_n20_n1# Gnd 0.93fF
C248 nand_0/gnd Gnd 0.32fF
C249 nand_0/vdd Gnd 0.04fF
C250 g1 Gnd 20.74fF
C251 p2 Gnd 20.85fF
C252 nand_0/w_n39_n8# Gnd 2.60fF

* Output
.control
tran 1n 200n
run
plot v(g1)
plot v(c2)
plot v(c3)
plot v(c4)
set curplottitle= "Srujana Vanka - 2020102005 - carry"
.endc
.end
```

Magic layout

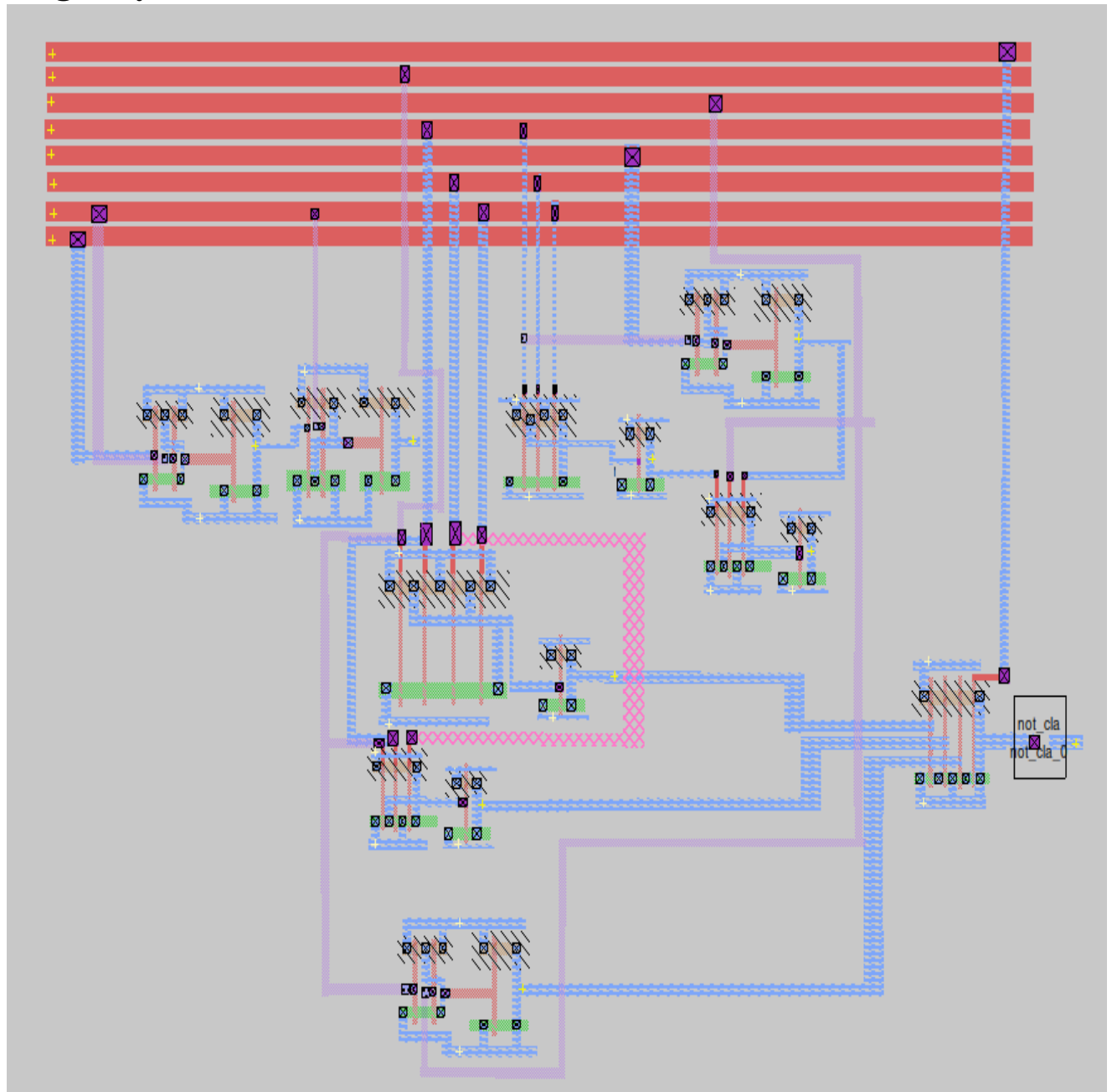

Sum block

Netlist

```
* SPICE3 file created from sum.ext - technology: scmos
*Sum block*

.include TSMC_180nm.txt

.param SUPPLY=1.8
.param LAMBDA=0.09u
.param w = {10*LAMBDA}
.param width_P={20*LAMBDA}
.param width_N={10*LAMBDA}
.global gnd vdd

vdd vdd gnd 'SUPPLY'

.option scale=0.09u

M1000 xor_cla_0/vdd xor_cla_0/a_25_n47# xor_cla_0/a_6_19#
xor_cla_0/w_n72_13# pfet w=19 l=4
+ ad=741 pd=154 as=361 ps=76
M1001 xor_cla_0/a_n61_n43# xor_cla_0/a_25_n47# xor_cla_0/gnd Gnd nfet w=12
l=4
+ ad=768 pd=200 as=228 ps=62
M1002 xor_cla_0/a_n40_n43# xor_cla_0/a_n22_n46# xor_cla_0/a_n40_19#
xor_cla_0/w_n72_13# pfet w=19 l=4
+ ad=380 pd=78 as=342 ps=74
M1003 xor_cla_0/a_n40_19# xor_cla_0/a_n49_n11# xor_cla_0/vdd
xor_cla_0/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1004 xor_cla_0/a_6_19# xor_cla_0/a_2_n49# xor_cla_0/a_n40_n43#
xor_cla_0/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1005 xor_cla_0/a_n61_n43# xor_cla_0/a_n22_n46# xor_cla_0/a_n40_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=216 ps=60
M1006 xor_cla_0/gnd xor_cla_0/a_2_n49# xor_cla_0/a_n61_n43# Gnd nfet w=12
l=4
```



```

+ ad=0 pd=0 as=0 ps=0
M1007 xor_cla_0/a_n40_n43# xor_cla_0/a_n49_n11# xor_cla_0/a_n61_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=0 ps=0
M1008 xor_cla_1/vdd xor_cla_1/a_25_n47# xor_cla_1/a_6_19#
xor_cla_1/w_n72_13# pfet w=19 l=4
+ ad=741 pd=154 as=361 ps=76
M1009 xor_cla_1/a_n61_n43# xor_cla_1/a_25_n47# xor_cla_1/gnd Gnd nfet w=12
l=4
+ ad=768 pd=200 as=228 ps=62
M1010 xor_cla_1/a_n40_n43# xor_cla_1/a_n22_n46# xor_cla_1/a_n40_19#
xor_cla_1/w_n72_13# pfet w=19 l=4
+ ad=380 pd=78 as=342 ps=74
M1011 xor_cla_1/a_n40_19# xor_cla_1/a_n49_n11# xor_cla_1/vdd
xor_cla_1/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1012 xor_cla_1/a_6_19# xor_cla_1/a_2_n49# xor_cla_1/a_n40_n43#
xor_cla_1/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0
M1013 xor_cla_1/a_n61_n43# xor_cla_1/a_n22_n46# xor_cla_1/a_n40_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=216 ps=60
M1014 xor_cla_1/gnd xor_cla_1/a_2_n49# xor_cla_1/a_n61_n43# Gnd nfet w=12
l=4
+ ad=0 pd=0 as=0 ps=0
M1015 xor_cla_1/a_n40_n43# xor_cla_1/a_n49_n11# xor_cla_1/a_n61_n43# Gnd
nfet w=12 l=4
+ ad=0 pd=0 as=0 ps=0
M1016 xor_cla_3/vdd xor_cla_3/a_25_n47# xor_cla_3/a_6_19#
xor_cla_3/w_n72_13# pfet w=19 l=4
+ ad=741 pd=154 as=361 ps=76
M1017 xor_cla_3/a_n61_n43# xor_cla_3/a_25_n47# xor_cla_3/gnd Gnd nfet w=12
l=4
+ ad=768 pd=200 as=228 ps=62
M1018 xor_cla_3/a_n40_n43# xor_cla_3/a_n22_n46# xor_cla_3/a_n40_19#
xor_cla_3/w_n72_13# pfet w=19 l=4
+ ad=380 pd=78 as=342 ps=74
M1019 xor_cla_3/a_n40_19# xor_cla_3/a_n49_n11# xor_cla_3/vdd
xor_cla_3/w_n72_13# pfet w=19 l=4
+ ad=0 pd=0 as=0 ps=0

```

```
M1020 xor_cla_3/a_6_19# xor_cla_3/a_2_n49# xor_cla_3/a_n40_n43#  
xor_cla_3/w_n72_13# pfet w=19 l=4  
+ ad=0 pd=0 as=0 ps=0  
M1021 xor_cla_3/a_n61_n43# xor_cla_3/a_n22_n46# xor_cla_3/a_n40_n43# Gnd  
nfet w=12 l=4  
+ ad=0 pd=0 as=216 ps=60  
M1022 xor_cla_3/gnd xor_cla_3/a_2_n49# xor_cla_3/a_n61_n43# Gnd nfet w=12  
l=4  
+ ad=0 pd=0 as=0 ps=0  
M1023 xor_cla_3/a_n40_n43# xor_cla_3/a_n49_n11# xor_cla_3/a_n61_n43# Gnd  
nfet w=12 l=4  
+ ad=0 pd=0 as=0 ps=0  
M1024 xor_cla_2/vdd xor_cla_2/a_25_n47# xor_cla_2/a_6_19#  
xor_cla_2/w_n72_13# pfet w=19 l=4  
+ ad=741 pd=154 as=361 ps=76  
M1025 xor_cla_2/a_n61_n43# xor_cla_2/a_25_n47# xor_cla_2/gnd Gnd nfet w=12  
l=4  
+ ad=768 pd=200 as=228 ps=62  
M1026 xor_cla_2/a_n40_n43# xor_cla_2/a_n22_n46# xor_cla_2/a_n40_19#  
xor_cla_2/w_n72_13# pfet w=19 l=4  
+ ad=380 pd=78 as=342 ps=74  
M1027 xor_cla_2/a_n40_19# xor_cla_2/a_n49_n11# xor_cla_2/vdd  
xor_cla_2/w_n72_13# pfet w=19 l=4  
+ ad=0 pd=0 as=0 ps=0  
M1028 xor_cla_2/a_6_19# xor_cla_2/a_2_n49# xor_cla_2/a_n40_n43#  
xor_cla_2/w_n72_13# pfet w=19 l=4  
+ ad=0 pd=0 as=0 ps=0  
M1029 xor_cla_2/a_n61_n43# xor_cla_2/a_n22_n46# xor_cla_2/a_n40_n43# Gnd  
nfet w=12 l=4  
+ ad=0 pd=0 as=216 ps=60  
M1030 xor_cla_2/gnd xor_cla_2/a_2_n49# xor_cla_2/a_n61_n43# Gnd nfet w=12  
l=4  
+ ad=0 pd=0 as=0 ps=0  
M1031 xor_cla_2/a_n40_n43# xor_cla_2/a_n49_n11# xor_cla_2/a_n61_n43# Gnd  
nfet w=12 l=4  
+ ad=0 pd=0 as=0 ps=0  
C0 xor_cla_3/a_n49_n11# xor_cla_3/w_n72_13# 0.11fF  
C1 xor_cla_3/a_n40_n43# xor_cla_3/a_25_n47# 0.25fF  
C2 xor_cla_2/a_n40_n43# xor_cla_2/a_n22_n46# 0.35fF  
C3 xor_cla_2/gnd xor_cla_2/a_n61_n43# 0.03fF
```

C4 xor_cla_0/w_n72_13# xor_cla_0/a_25_n47# 0.11fF
C5 xor_cla_1/a_n40_n43# xor_cla_1/w_n72_13# 0.03fF
C6 xor_cla_3/a_n40_n43# xor_cla_3/a_2_n49# 0.25fF
C7 xor_cla_2/a_n40_n43# xor_cla_2/a_n49_n11# 0.06fF
C8 xor_cla_0/w_n72_13# xor_cla_0/a_2_n49# 0.11fF
C9 xor_cla_1/a_n40_n43# xor_cla_1/a_25_n47# 0.25fF
C10 xor_cla_3/a_n40_n43# xor_cla_3/a_n22_n46# 0.35fF
C11 xor_cla_3/gnd xor_cla_3/a_n61_n43# 0.03fF
C12 xor_cla_2/a_n40_n43# xor_cla_2/w_n72_13# 0.03fF
C13 xor_cla_0/w_n72_13# xor_cla_0/a_n22_n46# 0.11fF
C14 xor_cla_1/a_n40_n43# xor_cla_1/a_2_n49# 0.25fF
C15 xor_cla_0/a_n40_n43# xor_cla_0/a_n49_n11# 0.06fF
C16 xor_cla_0/w_n72_13# xor_cla_0/vdd 0.05fF
C17 xor_cla_1/vdd xor_cla_1/w_n72_13# 0.05fF
C18 xor_cla_3/a_n40_n43# xor_cla_3/a_n49_n11# 0.06fF
C19 xor_cla_1/a_n40_n43# xor_cla_1/a_n22_n46# 0.35fF
C20 xor_cla_1/gnd xor_cla_1/a_n61_n43# 0.03fF
C21 xor_cla_1/a_25_n47# xor_cla_1/w_n72_13# 0.11fF
C22 xor_cla_3/a_n40_n43# xor_cla_3/w_n72_13# 0.03fF
C23 xor_cla_2/vdd xor_cla_2/w_n72_13# 0.05fF
C24 xor_cla_1/a_n40_n43# xor_cla_1/a_n49_n11# 0.06fF
C25 xor_cla_1/a_2_n49# xor_cla_1/w_n72_13# 0.11fF
C26 xor_cla_2/a_25_n47# xor_cla_2/w_n72_13# 0.11fF
C27 xor_cla_1/a_n22_n46# xor_cla_1/w_n72_13# 0.11fF
C28 xor_cla_3/vdd xor_cla_3/w_n72_13# 0.05fF
C29 xor_cla_0/a_25_n47# xor_cla_0/a_n40_n43# 0.25fF
C30 xor_cla_0/gnd xor_cla_0/a_n61_n43# 0.03fF
C31 xor_cla_2/a_2_n49# xor_cla_2/w_n72_13# 0.11fF
C32 xor_cla_1/a_n49_n11# xor_cla_1/w_n72_13# 0.11fF
C33 xor_cla_3/a_25_n47# xor_cla_3/w_n72_13# 0.11fF
C34 xor_cla_0/a_2_n49# xor_cla_0/a_n40_n43# 0.25fF
C35 xor_cla_2/a_n22_n46# xor_cla_2/w_n72_13# 0.11fF
C36 xor_cla_0/w_n72_13# xor_cla_0/a_n49_n11# 0.11fF
C37 xor_cla_3/a_2_n49# xor_cla_3/w_n72_13# 0.11fF
C38 xor_cla_0/a_n40_n43# xor_cla_0/a_n22_n46# 0.35fF
C39 xor_cla_2/a_n49_n11# xor_cla_2/w_n72_13# 0.11fF
C40 xor_cla_2/a_n40_n43# xor_cla_2/a_25_n47# 0.25fF
C41 xor_cla_3/a_n22_n46# xor_cla_3/w_n72_13# 0.11fF
C42 xor_cla_2/a_n40_n43# xor_cla_2/a_2_n49# 0.25fF
C43 xor_cla_0/w_n72_13# xor_cla_0/a_n40_n43# 0.03fF

```
C44 xor_cla_2/gnd Gnd 0.17fF
C45 xor_cla_2/a_n61_n43# Gnd 0.91fF
C46 xor_cla_2/a_n40_n43# Gnd 0.62fF
C47 xor_cla_2/vdd Gnd 0.63fF
C48 xor_cla_2/a_25_n47# Gnd 0.47fF
C49 xor_cla_2/a_2_n49# Gnd 0.49fF
C50 xor_cla_2/a_n22_n46# Gnd 0.47fF
C51 xor_cla_2/a_n49_n11# Gnd 0.46fF
C52 xor_cla_2/w_n72_13# Gnd 4.05fF
C53 xor_cla_3/gnd Gnd 0.17fF
C54 xor_cla_3/a_n61_n43# Gnd 0.91fF
C55 xor_cla_3/a_n40_n43# Gnd 0.62fF
C56 xor_cla_3/vdd Gnd 0.63fF
C57 xor_cla_3/a_25_n47# Gnd 0.47fF
C58 xor_cla_3/a_2_n49# Gnd 0.49fF
C59 xor_cla_3/a_n22_n46# Gnd 0.47fF
C60 xor_cla_3/a_n49_n11# Gnd 0.46fF
C61 xor_cla_3/w_n72_13# Gnd 4.05fF
C62 xor_cla_1/gnd Gnd 0.17fF
C63 xor_cla_1/a_n61_n43# Gnd 0.91fF
C64 xor_cla_1/a_n40_n43# Gnd 0.62fF
C65 xor_cla_1/vdd Gnd 0.63fF
C66 xor_cla_1/a_25_n47# Gnd 0.47fF
C67 xor_cla_1/a_2_n49# Gnd 0.49fF
C68 xor_cla_1/a_n22_n46# Gnd 0.47fF
C69 xor_cla_1/a_n49_n11# Gnd 0.46fF
C70 xor_cla_1/w_n72_13# Gnd 4.05fF
C71 xor_cla_0/gnd Gnd 0.17fF
C72 xor_cla_0/a_n61_n43# Gnd 0.91fF
C73 xor_cla_0/a_n40_n43# Gnd 0.62fF
C74 xor_cla_0/vdd Gnd 0.63fF
C75 xor_cla_0/a_25_n47# Gnd 0.47fF
C76 xor_cla_0/a_2_n49# Gnd 0.49fF
C77 xor_cla_0/a_n22_n46# Gnd 0.47fF
C78 xor_cla_0/a_n49_n11# Gnd 0.46fF
C79 xor_cla_0/w_n72_13# Gnd 4.05fF
```

```
* Output
```

```
.control
```


```
tran 1n 200n
```

```

run
plot v(c1) v(c2) v(c3) v(c4)
set curplotttitle= "Srujana Vanka - 2020102005 - PGblock"
.endc
.end

```

Magic layout

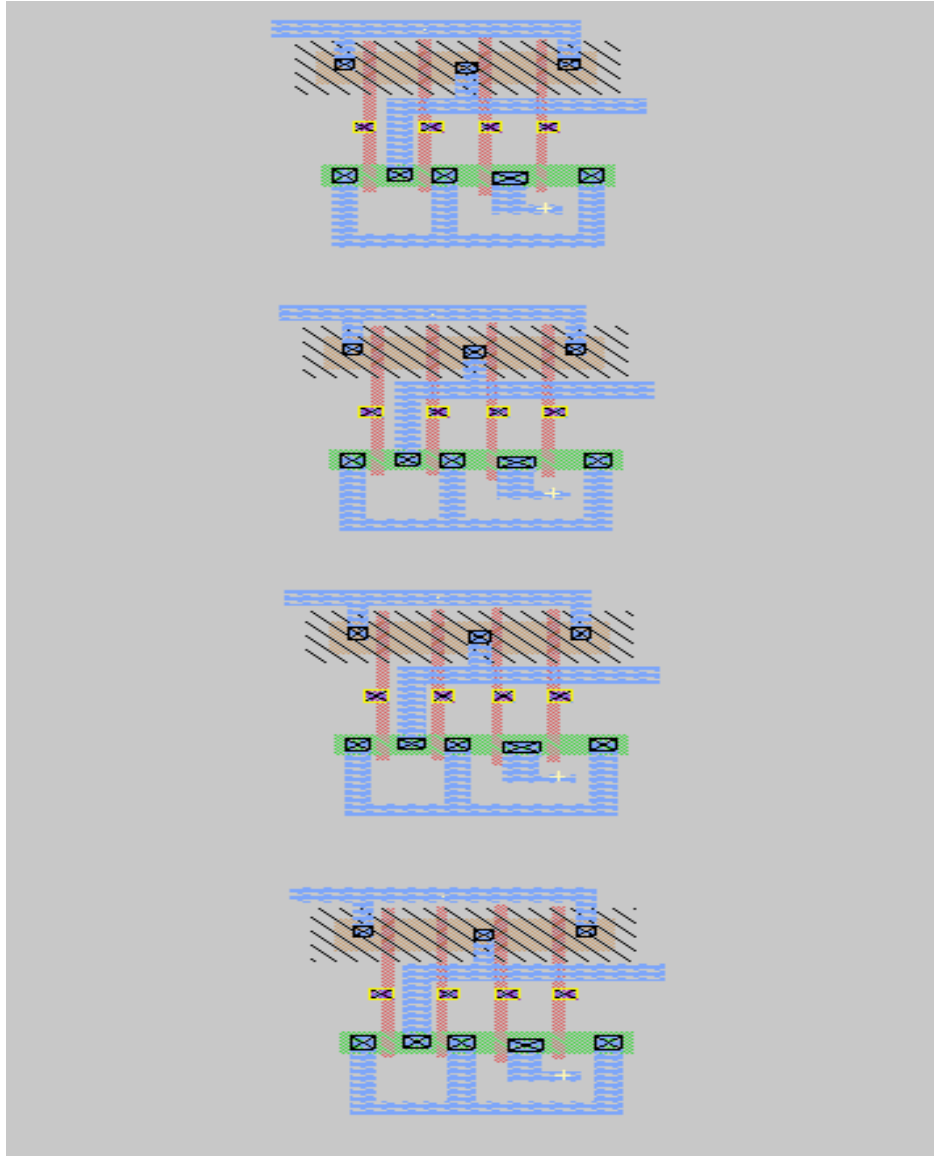

Question 9

Delays:

	Prelayout	Post layout
Sum/Propagate	0.026ns	0.029ns
Generate	0.041ns	0.069ns
Carry	0.24ns	0.29ns

	Pre layout	Post layout
ALL BLOCKS	0.61ns	0.93ns

Question 10

Using Verilog HDL to write the structural description

```
module CLA_Adder(cin,a1,a2,a3,a4,b1,b2,b3,b4,s1,s2,s3,s4,cout) ;
input cin,a1,a2,a3,a4,b1,b2,b3,b4;
output s1,s2,s3,s4,cout;
wire p1,p2,p3,p4,g1,g2,g3,g4,t1,t2,t3,t4,t5,t6;

// propagate and generate
xor #1 (p1,a1,b1);
xor #2 (p2,a2,b2);
xor #3 (p3,a3,b3);
xor #4 (p4,a4,b4);

and #1 (g1,a1,b1);
and #2 (g2,a2,b2);
```

```

and #3 (g3,a3,b3);
and #4 (g4,a4,b4);

// carry
// c1
and #5 (t1, p1, cin);
or #1 (c1, g1, t1);

// c2
and #6 (t2, p1, p2, cin);
and #7 (t3, g1, p2);
or #2 (c2, t2, t3, g1);

// c3
and #8 (t4, p1, p2, p3, cin);
and #9 (t5, g1, p2, p3);
and #10 (t6, g2, p3);
or #3 (c3, g2, t6, t5, t4);

// c4
and #11 (t7, p1, p2, p3, p4, cin);
and #12 (t8, g1, p2, p3, p4);
and #13(t9, g2, p3, p4);
and #14(t10, g3, p4);
or #4 (c4, g3, t10, t9, t8, t7);

// sum
xor #5 (s1,p1,c1);
xor #6 (s2,p2,c2);
xor #7 (s3,p3,c3);
xor #8 (s4,p4,c4);

endmodule

```

Testbench

```

module testbench;
reg cin,a1,a2,a3,a4,b1,b2,b3,b4;
wire s1,s2,s3,s4,c5;
CLA_Adder DUT(cin,a1,a2,a3,a4,b1,b2,b3,b4,s1,s2,s3,s4,cout);

```

```

initial begin
$dumpfile("cla.vcd");
$dumpvars(0,testbench);
//print statement
$monitor($time," A=%b%b%b%b B=%b%b%b%b Cout=%b
S=%b%b%b%b",a4,a3,a2,a1,b4,b3,b2,b1,cout,s4,s3,s2,s1);

    cin = 1'b1;
    a1 = 1'b1;
    b1 = 1'b1;
    a2 = 1'b1;
    b2 = 1'b1;
    a3 = 1'b1;
    b3 = 1'b1;
    a4 = 1'b1;
    b4 = 1'b1;

    #2560 $finish;
end
always #5 a1 = ~a1;
always #10 b1 = ~b1;
always #20 a2 = ~a2;
always #40 b2 = ~b2;
always #80 a3 = ~a3;
always #160 b3 = ~b3;
always #320 a4 = ~a4;
always #640 b4 = ~b4;
always #1280 cin = ~cin;
endmodule

```

Waveform

